design ideas

GMR sensors manage batteries

D Ramirez and J Pelegri, University of Valencia, Spain

HE PAST FEW decades have seen remarkable progress in magnetic-sensor technology. Early and current sensors exploit the Hall effect; more recent devices use an effect called giant magnetoresistance (GMR). GMR sensors use semiconductor processing of materials such as indium-antimony. The GMR sensor in Figure 1 comprises four GMR resistors in a Wheatstone-bridge configuration. Two arms of the bridge have active resistors; the other two resis-


tors are shielded against magnetic fields. When a magnetic field impinges on the sensor, the GMR effect decreases the resistance of the active pair of resistors, and the values of the shielded pair remain constant. GMR-based semiconductors are suitable for current measurement because they respond to the magnetic field rising from the current. However, in this application, the Wheatstone-bridge topology allows you to measure and control power.

er pins of the GMR sensor to the voltage


terminal, V+, and place the cable or trace the battery current traverses near the sensor. The output voltage of the bridge then relates to the power, which is the product of V+ and the current. The circuit in Figure 1 provides a way to check a battery's condition. Measuring a battery's voltage is not the best way to check its condition; it's better to measure the power that the battery delivers in a discharge process to evaluate the battery's energy capacity and life. The circuit in Figure 1 discharges a battery in a constant-power mode. You can select the level of discharge power. The GMR sensor's output signal is related to the discharge power. The power stage uses a bipolar Darlington transistor, which draws little power from its op-amp driver. You place the GMR sensor over the pc-board trace

Using the GMR sensor in a negativefeedback closed loop, the circuit controls the battery discharge in constant-power

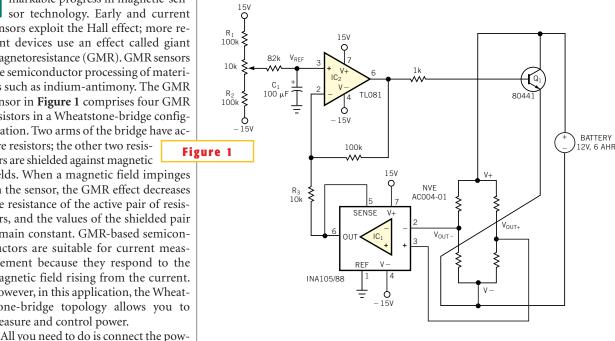that connects the Darlington's emitter to



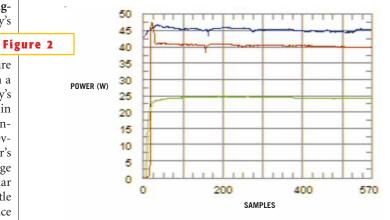A GMR sensor and a closed-loop regulation circuit provide a constant-power discharge process for measuring a battery's energy capacity and life.




Sampling shows constant-power discharge profiles at 25, 40, and 45W for Figure 1's battery-management circuit.

mode. The difference amplifier (IC,) converts the sensor's differential output signal to a unipolar signal; the op amp, IC, supplies the appropriate loop gain and compares the difference-amplifier output with the externally selected ref-

designideas

erence voltage. IC₂ provides the base current for the Darlington transistor, which discharges the battery at a constant-power rate. Figure 2 shows profiles of the constant-power battery discharge. Figure 3 shows current, voltage, and power profiles of the constant-power discharge process. When the battery voltage decreases, the current discharge increases, and the power remains constant. (DI #2394).

To Vote For This Design, Circle No. 339

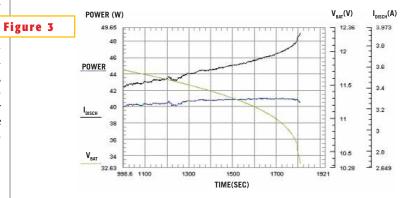

To provide constant-power discharge, the battery's voltage and current profiles have reciprocal, mirror-image slopes.