

Limited Warranty and Liability

Information in this document is believed to be accurate and reliable. However, NVE does not give any representations or warranties, expressed or implied, as to the accuracy or completeness of such information and shall have no liability for the consequences of use of such information. In no event shall NVE be liable for any indirect, incidental, punitive, special or consequential damages (including, without limitation, lost profits, lost savings, business interruption, costs related to the removal or replacement of any products or rework charges) whether or not such damages are based on tort (including negligence), warranty, breach of contract or any other legal theory.

Right to Make Changes

NVE reserves the right to make changes to information published in this document including, without limitation, specifications and product descriptions at any time and without notice.

Use in Life-Critical or Safety-Critical Applications

Unless NVE and a customer explicitly agree otherwise in writing, NVE products are not designed, authorized or warranted to be suitable for use in life support, life-critical or safety-critical devices or equipment. NVE accepts no liability for inclusion or use of NVE products in such applications and such inclusion or use is at the customer's own risk. Should the customer use NVE products for such application whether authorized by NVE or not, the customer shall indemnify and hold NVE harmless against all claims and damages.

Applications

Applications described in this document are illustrative only. NVE makes no representation or warranty that such applications will be suitable for the specified use without further testing or modification. Customers are responsible for the design and operation of their applications and products using NVE products, and NVE accepts no liability for any assistance with applications or customer product design. It is customer's sole responsibility to determine whether the NVE product is suitable and fit for the customer's applications and products planned, as well as for the planned application and use of customer's third party customers. Customers should provide appropriate design and operating safeguards to minimize the risks associated with their applications and products. NVE does not accept any liability related to any default, damage, costs or problem which is based on any weakness or default in the customer's applications or products, or the application or use by customer's third party customers. The customer is responsible for all necessary testing for the customer's applications and products using NVE products in order to avoid a default of the applications and the products or of the application or use by customer's third party customers. NVE accepts no liability in this respect.

An ISO 9001 Certified Company

NVE Corporation
11409 Valley View Road
Eden Prairie, MN 55344-3617


©NVE Corporation

All rights are reserved. Reproduction in whole or in part is prohibited without the prior written consent of the copyright owner.

Manual No.: SB-00-150 revision A



AG974-07E

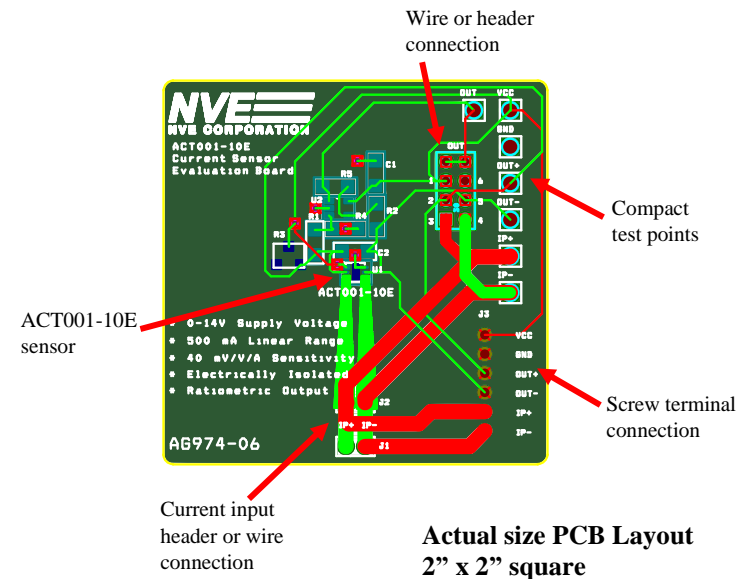ACT001-10E Isolated Current Sensor Evaluation Board



Overview

This evaluation board allows you to test the remarkable ACT001-10E current sensor and a common application circuit. The ACT001-10E is a fully-isolated, inline current sensor with an on-chip current strap. A Wheatstone bridge manufactured with NVE's state-of-the-art tunneling magnetoresistance (TMR) sensor elements detects the magnetic field from the input current across NVE's unique polymer isolation barrier.

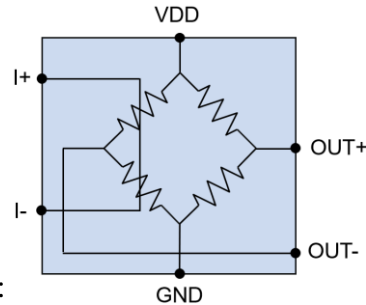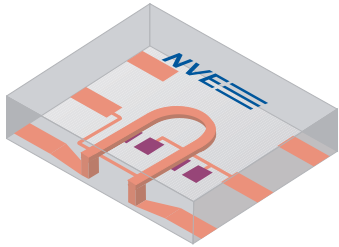

Key ACT001-10E features include:


- Bipolar Wheatstone bridge analog output
- High Sensitivity: 0.04 mV/V/mA typical
- Excellent linearity over wide range: 1% full-scale over ± 500 mA
- 15 k Ω bridge resistance/7.5 k Ω output impedance for easy interface
- Low hysteresis: 1% worst case
- Wide bandwidth: 300 kHz
- -40 °C to 125 °C
- Ultraminiature 2.5 mm x 2.5 mm TDFN6 package

More information can be found in the datasheet, available for download at www.nve.com/Downloads/ACT001.pdf

Quick Start

- ⇒ Connect V_{cc} and GND to a power supply (2.7 to 14V) or a battery.
- ⇒ Connect the sensor "Out+" and "Out-" to a meter.
- ⇒ Connect an AC or DC current via the IP+ and IP- terminals.
- ⇒ Compare the sensor output to the current.

Schematic

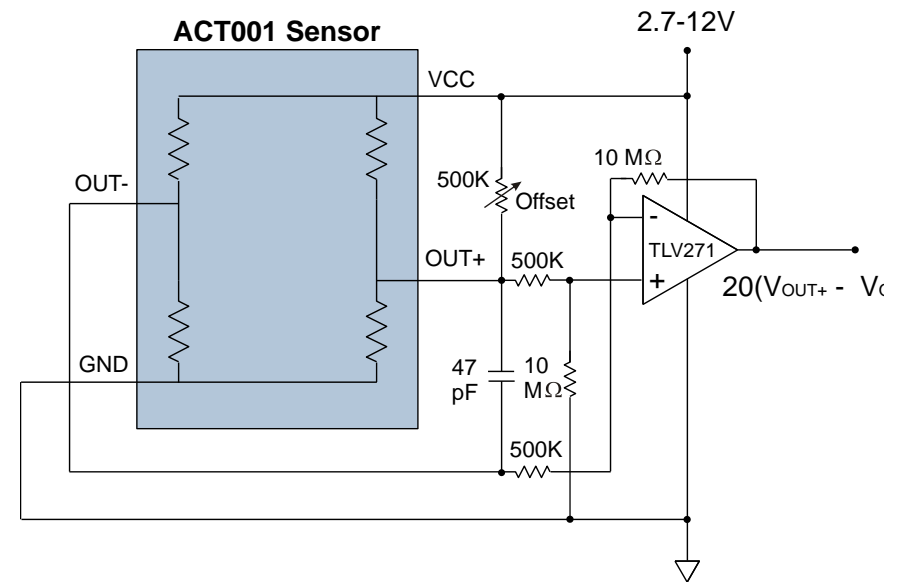

This op-amp circuit has a gain of 20 for full-scale at approximately the sensor's maximum output. The potentiometer provides a positive offset so negative currents still produce a positive output, and corrects the sensor's offset. The 500 k Ω input resistors are significantly higher than the sensor output impedance to avoid loading. The capacitor limits high-frequency noise. The low-cost, low bias current op amp allows large resistors to avoid loading the sensor bridge.

Customer Support

Applications support: sensor-apps@nve.com

Ordering and purchasing information: orders@nve.com

Web-app design support: www.nve.com/spec/calculators

Application notes: www.nve.com/SensorApps

YouTube video support: youtube.com/c/NveCorporation